



## INTRODUCTION

**Transistor** - It is just a **switch**. It is either switched **on** (current can flow), or switched **off** (no current flow)




**Gate** - A device that performs basic operation on electrical signals

**Circuits** - Gates combined to perform more complicated tasks

**Logic diagrams** - A graphical representation of a circuit; each gate has its own symbol


**Truth tables** - A table showing all possible input value and the associated output values

 **Boolean expressions** - Uses Boolean algebra, a mathematical notation for expressing two-valued logic


 
## INTRODUCTION

- Digital systems are concerned with digital signals.
- **Binary signals** are the most common form of digital signals. They can be used individually to represent a single binary quantity or the state of a single switch.




A simple binary arrangement

S	L
OPEN	OFF
CLOSED	ON


S	L
0	0
1	1

truth table

 

 
## INTRODUCTION

- The building blocks used to create digital circuits are **logic gates**.
- The name is derived from the ability of such a device to **make decisions**. They produce a logic-1 or logic-0 output signal, if input logic requirements are satisfied.
- In most logic gates, the **low (0)** state is approximately zero volts (0 V), while the **high (1)** state is approximately five volts positive (+5 V).
- Most logic gates have **two inputs and one output**. There are seven basic logic gates: **AND, OR, NOT, NAND, NOR, XOR, and XNOR**.
- Each gate has its own **logic symbol** which allows complex functions to be represented by a logic diagram.
- The function of each gate can be represented by a **truth table** or using **Boolean notation**.



 
# LOGIC GATES

- ◆ Inverter (NOT Gate)
- ◆ AND Gate
- ◆ OR Gate
- ◆ Exclusive-OR (XOR) Gate
- ◆ NAND Gate = AND Gate + Inverter
- ◆ NOR Gate = OR Gate + Inverter
- ◆ Exclusive-NOR Gate = XOR Gate + Inverter



## Inverter (NOT) Gate

The NOT gate (or inverter)

 

(a) Circuit symbol


A	B
0	1
1	0

(b) Truth table


$$B = A' \text{ or } B = \sim A \text{ or}$$

$$B = \bar{A}$$


(c) Boolean expression

 

(d) Timing Diagram

 

(e) IEEE Symbol

 

Effect of Double Inversion

X	$\sim X$	$\sim \sim X$
0	1	0
1	0	1

# Buffer Gate



(a) Circuit symbol


A	B
0	0
1	1

(b) Truth table

$$B = A$$

(c) Boolean expression

# AND Gate

 


(a) Circuit symbol

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1


(b) Truth table

$$C = A \cdot B$$

(c) Boolean expression

 

(d) Timing Diagram

 

(e) IEEE Symbol

# OR Gate

## The OR gate




(a) Circuit symbol

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1


(b) Truth table

$$C = A + B$$

(c) Boolean expression

 


(d) Timing Diagram

 


(e) IEEE Symbol

# BASIC LOGIC GATES

 

AND	OR	NOT
Two or more inputs but only one output	Two or more inputs but only one output.	One input, one output; Unary operation
Algebraic Function: $Y = A.B$ Logical Multiplication	Algebraic Function: $Y = A+B$ Logical Addition	Algebraic Function: $Y = A'$ Complement
<b>All or nothing gate</b> <b>Output is 1, if and only if all its inputs are 1.</b>	<b>Any or all gate</b> <b>Output is LOW only when all of the inputs are LOW.</b>	<b>Inverter gate</b>

# NAND Gate

 


(a) Circuit symbol

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0


(b) Truth table

$$C = \overline{A \cdot B}$$

(c) Boolean expression

 


(d) Timing Diagram

 

(e) IEEE Symbol

# NOR Gate

The NOR gate

 


(a) Circuit symbol

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0


(b) Truth table

$$C = \overline{A + B}$$

(c) Boolean expression

 

(d) Timing Diagram

 


(e) IEEE Symbol

# XOR Gate

"Odd but not even gate"

## The Exclusive OR gate

 

(a) Circuit symbol


A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

(b) Truth table


$$C = A \oplus B$$

$$= \bar{A}B + A\bar{B}$$

(c) Boolean expression

 

(d) Timing Diagram

 

(e) IEEE Symbol

Complement of a variable is represented by an overbar or ' Thus, complement of variable B is represented as B'.

# XNOR Gate

## The Exclusive NOR gate




(a) Circuit symbol

A	B	C
0	0	1
0	1	0
1	0	0
1	1	1


(b) Truth table

$$C = \overline{A \oplus B}$$

(c) Boolean expression

 


(d) Timing Diagram

 

(e) IEEE Symbol

# DERIVED LOGIC GATES

 

NAND	NOR	XOR	XNOR
Not AND	NOT OR	Odd, but not even gate; HIGH when odd no. of HIGH inputs	Exclusive NOR gate; Inverted XOR gate
Algebraic Function: $Y = (A.B)'$	Algebraic Function: $Y = (A+B)'$	Algebraic Function: $Y = A'B + AB'$	Algebraic Function: $Y = AB + A'B'$
The unique output from the NAND gate is 0 only when all inputs are 1.	The unique output from the NOR gate is 1 only when all inputs are 0.	<b>Anticoincidence gate/inequality detector</b> - produces an output 1 only when the inputs are not equal	<b>coincidence gate/equality detector</b> - since produces an output 1 only when the inputs are equal


## QUIZ

1. How many AND gates are required to realize  $Y = CD + EF + G$ ?

- a) 4
- b) 5
- c) 3
- d) 2


2. The NOR gate output will be high if the two inputs are

- a) 00
- b) 01
- c) 10
- d) 11

 



# QUIZ

 


3. An OR gate has 4 inputs. One input is high and the other three are low. The output is .....

- a) Low
- b) High
- c) alternately high and low
- d) may be high or low depending on relative magnitude of inputs

4. How many two input AND gates and two input OR gates are required to realize  $Y = ST + PQ + RS$ ?

- a) 3, 2
- b) 4, 2
- c) 1, 1
- d) 2, 3

# QUIZ

 

5. The symbol  $\begin{matrix} A \\ B \end{matrix} \begin{matrix} \boxed{\geq 1} \end{matrix} X$  is for

- a. OR gate
- b. AND gate
- c. NOR gate
- d. XOR gate

6. Function of NOT gate is to .....

- a) Stop signal
- b) Invert input signal
- c) Act as a universal gate
- d) None of the above